

**MS101 Makerspace**  
**2022-23/II Spring**  
**Expt 2: DC Power Supply (Ver 1.1)**

**Objectives:**

- i) To measure and compare the ripple voltages of half and full wave (bridge) rectifiers.
- ii) To compare the output voltage variations and output resistances of the bridge rectifier based DC power supply with that of an IC regulator based DC power supply.

**List of components:**

Step-down transformer (230 V/0-12 V), IN4007 diodes, electrolytic capacitors, resistors, and LM 7805 IC.

**Important note:**

**This experiment is a very basic one, but a dangerous one too. You need to be extremely careful with your wiring. Incorrect connections of the diodes and/or the electrolytic capacitors can result in explosion and fire. You might severely damage your bread board too. Please note the following:**

- i) **Electrolytic capacitors used in circuits of Fig.1.3 and Fig. 2.3 have polarity, i.e. the capacitors have '+' and '-' terminals. If the electrolytic capacitor is connected with the wrong polarity, it may explode and may cause fire/injury.**
- ii) **Similarly, the diodes have anode and cathode terminals, which need to be connected correctly. Wrong connections can result in the diode or the transformer burning. Once again careless wiring of the diodes may result in injury.**
- iii) **In order to avoid the above dangerous scenarios, you must get your circuit tested by your TA before switching ON power to the transformer. Also, while making changes, such as changing the C value from 100  $\mu$ F to 1000  $\mu$ F, be sure to first switch OFF power to the transformer, and then connect the capacitor once again observing the correct polarity. Get your connection ok-ed by your TA and then only switch ON the power. Similarly, it is best to switch OFF power to the transformer while changing the  $R_L$  values.**

**Part A – Unregulated DC Power Supply using Half-wave Rectifier Circuit and a Capacitor Filter**

**1.1 Half-wave Rectifier**

The circuit diagram of a half-wave rectifier circuit is shown below. We will be using a 230 V/0-12 V step-down transformer and an IN4007 diode (peak forward current: 1A, peak-inverse voltage: 1000 V) to realize the circuit. As shown in the diode image, the cathode lead is identified by the band close to it.

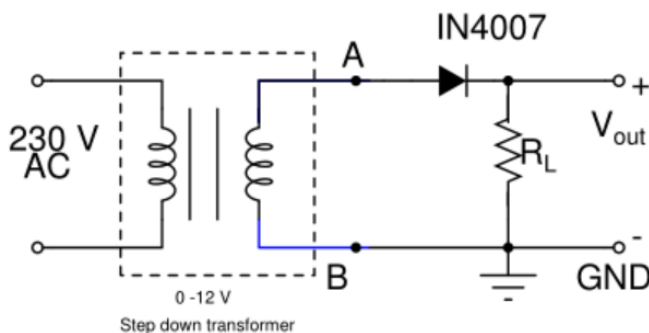


Fig 1.1 Half-wave rectifier circuit

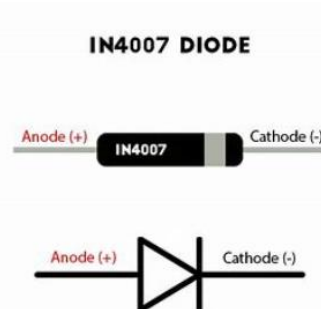


Fig. 1.2 IN4007 diode image

### Experiment:

- Wire the half-wave rectifier circuit neatly and carefully on the breadboard.  $R_L = 1\text{ k}\Omega$ . **Take extra care in wiring the diode and the load resistance correctly.**
- Connect CH-1 of the DSO to the transformer output (the voltage  $V_{AB}$ ) and CH-2 to the rectifier output ( $V_{out}$ ).

### Note:

- Take extra care to avoid shock. The primary side of the transformer has already been insulated and connected to a plug. You should use only the two leads of the transformer secondary for circuit connections, i.e. points A and B shown in Fig.1.1.
- For getting a stable display in CH-1 and CH-2, it is best to use 'AC Line' as the trigger source. (Use: Trigger Menu > Source > AC Line)

### Observation and Measurement:

- Sketch the  $V_{AB}$  and  $V_{out}$  waveforms and note down their peak-to-peak voltages.
- After step (a), switch-OFF power to the transformer.

## 1.2 Half-wave Rectifier Circuit with a Capacitor Filter

The half-wave rectifier circuit of Fig. 1.1 is modified and re-drawn in Fig.1.3. In the modified circuit, a large value capacitor ( $1000\text{ }\mu\text{F}$ ) is connected across  $R_L$ . Please note from Fig.1.2 the '-' terminal of the capacitor (the '-' terminal is generally the one with the shorter lead length).

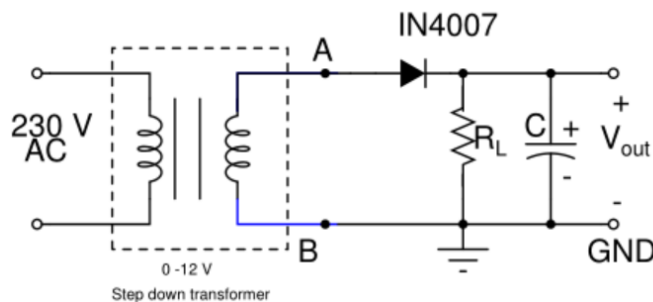


Fig 1.3 Half-wave rectifier circuit with a capacitor filter

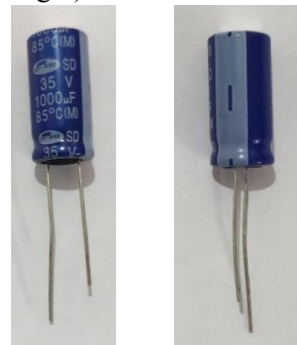


Fig. 1.4 Images of the  $1000\text{ }\mu\text{F}$  capacitor

### Experiment:

- Switch-OFF power to the transformer. Modify the circuit of Fig.1.1 so as to connect the  $1000\text{ }\mu\text{F}$  electrolytic capacitor  $C$  across  $R_L$ . **Take extreme care to see that '-' terminal of the electrolytic capacitor is connected to the GND and the '+' terminal to  $V_{out}$ .**
- Switch ON power to the transformer.

### Observation and Measurement:

- Sketch the  $V_{AB}$  and  $V_{out}$  waveforms for the following values
  - $R_L = 1\text{ k}\Omega$ ,  $C = 1000\text{ }\mu\text{F}$ .
  - For the above case, note down the peak-to-peak ripple voltage and the mean value of  $V_{out}$ . (Use the 'Measure' feature of the DSO to obtain the mean value of  $V_{out}$ ). Please also use your DMM to measure  $V_{out}$ . For this measurement the DMM should be in the DC voltage setting.

*Note: Peak-to-peak ripple voltage is relatively much smaller compared to the mean value of  $V_{out}$  (say  $0.5\text{ V}$  of ripple riding over  $16$  or  $17\text{ V DC}$ ). In order to measure the small ripple voltage correctly, you should put the DSO channel to the **AC mode** and choose an appropriate scale.*

## Part B – Unregulated DC Power Supply using the Bridge Rectifier Circuit and a Capacitor Filter

### 2.1 Bridge Rectifier Circuit

Circuit diagram of the bridge rectifier circuit is shown below. We will be using the same 230 V/0-12 V step-down transformer of Part A. In addition, we will use four IN4007 diodes (peak forward current: 1A, peak-inverse voltage: 1000 V) to realize the circuit. As shown in the diode image (see Fig.2.2), the cathode lead is identified by the band close to it.

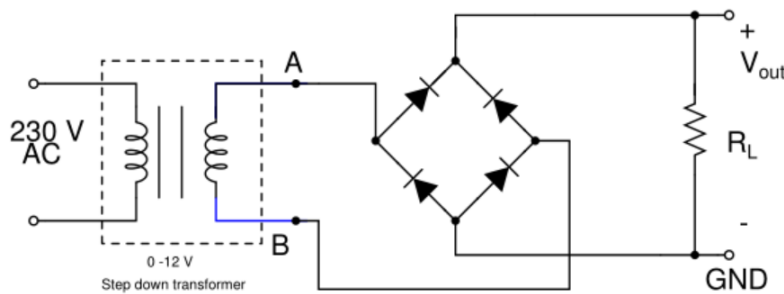


Fig 2.1 Bridge rectifier circuit

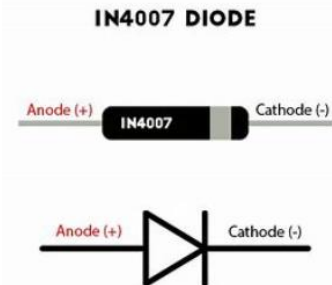


Fig. 2.2 IN4007 diode image

#### Experiment:

- Wire the bridge rectifier circuit neatly and carefully on the breadboard.  $R_L = 10\text{ k}\Omega$ . Take extra care in wiring the diodes correctly with the right polarity as shown. **Please note even though the wire from output B of the transformer is crossing the GND line, there is no connection there.**
- Connect DSO (CH-1 or CH-2) only to the rectifier output ( $V_{out}$ ). Do not connect any DSO probe to the transformer secondary outputs A or B. (i.e., do not try to display  $V_{AB}$  on the DSO). This will result the transformer secondary getting shorted through one of the diodes.**

#### Note:

- For getting a stable display in **CH-1 or CH-2**, it is best to use 'AC Line' as the trigger source. (Use: Trigger Menu > Source > AC Line)

#### Observation and Measurement:

- Sketch the  $V_{out}$  waveform (for  $R_L = 10\text{ k}\Omega$ ) and the peak-to-peak voltage.
- After completing (a), switch-OFF power to the transformer.

### 1.3 Bridge Rectifier Circuit with a Capacitor Filter

The bridge rectifier circuit of Fig.2.1 is modified and re-drawn in Fig.2.3. In the modified circuit, a large value capacitor (100  $\mu\text{F}$  or 1000  $\mu\text{F}$ ) is connected across  $R_L$ .

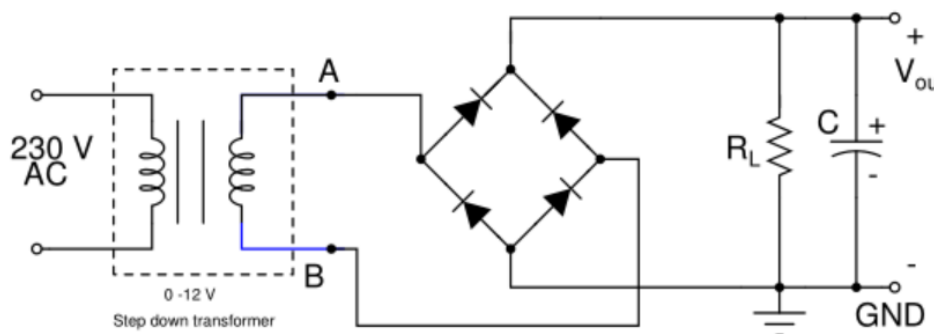


Fig 2.3 Bridge rectifier circuit with a capacitor filter

### Experiment:

- i) Switch-OFF power to the transformer. Modify the circuit of Fig. 2.1 so as to connect the 100  $\mu\text{F}$  electrolytic capacitor C across  $R_L$ . **Take extreme care to see that ‘-’ terminal of the electrolytic capacitor is connected to the GND and the ‘+’ terminal to  $V_{out}$ .**
- ii) Switch ON power to the transformer.

### Observation and Measurement:

Sketch the  $V_{out}$  waveforms for the following values

- i)  $R_L = 10\text{ k}\Omega$ ,  $C = 100\text{ }\mu\text{F}$ .
- ii)  $R_L = 3.3\text{ k}\Omega$ ,  $C = 100\text{ }\mu\text{F}$ .
- iii)  $R_L = 1\text{ k}\Omega$ ,  $C = 100\text{ }\mu\text{F}$ .

- For each of the above cases, note down the peak-to-peak ripple voltage and the mean value of  $V_{out}$  ( $= V_{out\text{-mean}}$ ). Use the ‘Measure’ feature of the DSO to obtain  $V_{out\text{-mean}}$ . Use also your DMM to measure  $V_{out}$ . For this measurement the DMM should be in the DC voltage setting.
- Determine the output resistance of the bridge rectifier power supply (with capacitive filter).  
Output resistance  $= |\Delta V_{out} / \Delta I_L|$ .  
 $\Delta V_{out} = (V_{out\text{-mean}} \text{ for } R_L = 10\text{ k}\Omega) - (V_{out\text{-mean}} \text{ for } R_L = 1\text{ k}\Omega)$ .  $\Delta I_L$  is the currents for these cases.  
For example,  $I_L$  (for  $R_L = 10\text{ k}\Omega$ )  $= V_{out\text{-mean}} / 10\text{ k}\Omega$ . Similarly find  $I_L$  for  $R_L = 1\text{ k}\Omega$ .

- b) Switch-OFF power to the transformer. **Change C to 1000  $\mu\text{F}$ , once again ensuring that ‘-’ of the electrolytic capacitor is connected to the GND and the ‘+’ terminal to  $V_{out}$ .**

Switch ON power to the transformer. Observe and sketch the  $V_{out}$  waveforms for the following values

- i)  $R_L = 10\text{ k}\Omega$ ,  $C = 1000\text{ }\mu\text{F}$ .
- ii)  $R_L = 3.3\text{ k}\Omega$ ,  $C = 1000\text{ }\mu\text{F}$ .
- iii)  $R_L = 1\text{ k}\Omega$ ,  $C = 1000\text{ }\mu\text{F}$ .

- For each of the above cases, note down the peak-to-peak ripple voltage and the mean value of  $V_{out}$  ( $= V_{out\text{-mean}}$ ).
- Determine the output resistance of the above power supply.  
Output resistance  $= |\Delta V_{out} / \Delta I_L|$ . Use the method as was described earlier to determine  $\Delta V_{out}$  and  $\Delta I_L$ .
- Compare the output resistance of the bridge rectifier with  $C = 100\text{ }\mu\text{F}$  with the case when  $C = 1000\text{ }\mu\text{F}$ . Which case is better? Justify your answer.

## Part C – IC Regulator (LM 7805)

We shall use a very commonly used three-terminal 5V regulator IC to realize a regulated DC power supply. This regulator IC is capable of giving a constant  $V_{out}$  ( $= 5\text{ V}$ ) for a large range of  $V_{in}$  (for  $V_{in}$  varying from  $7\text{ V}$  to  $25\text{ V}$ ). Also,  $V_{out}$  will be a constant for a large range of  $I_L$  (for  $I_L$  varying from  $0$  to  $1\text{ A}$ ).

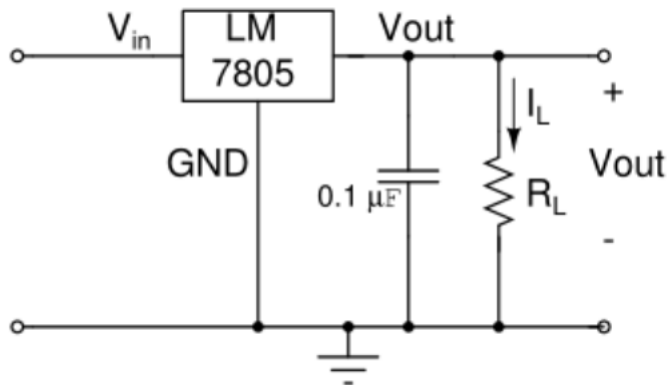


Fig. 3.1 7805 regulator circuit



Fig. 3.2 LM7805 IC image

### Part C.1 – Measurement of Output Voltage Fluctuations with Load Currents (Output Resistance)

Circuit values: LM7805,  $0.1\text{ }\mu\text{F}$  ;  $R_L = 680\text{ }\Omega$ ,  $1\text{ k}\Omega$ , and  $3.3\text{ k}\Omega$

$V_{in}$  (of LM7805) =  $V_{out}$  of the Bridge rectifier circuit of Fig. 2.3 with  $R_L$  removed and  $C = 1000\text{ }\mu\text{F}$ ;

For measuring output resistance of the LM7805 IC, we need to vary the load currents while keeping  $V_{in}$  to the circuit at a constant value. The output resistance is indicative of the load regulation of LM7805.

#### Experiment:

1. Wire the circuit of Fig.3.1. Identify the  $V_{in}$ ,  $GND$  and  $V_{out}$  pins of the LM7805 and take special care to connect the three terminals correctly. The IC terminals may be thicker compared to other components; hence you need to insert the pins carefully. Also, connect the  $0.1\text{ }\mu\text{F}$  ceramic capacitor as shown.
2. We shall use the output of the Bridge rectifier (circuit shown in Fig.2.3, but with  $R_L$  removed and  $C = 1000\text{ }\mu\text{F}$ ) as  $V_{in}$  to the LM 7805 regulator IC.
3. Vary  $R_L$  values:  $680\text{ }\Omega$ ,  $820\text{ }\Omega$ ,  $1\text{ k}\Omega$ ,  $2.2\text{ k}\Omega$  and  $3.9\text{ k}\Omega$ . For each  $R_L$  value, measure  $V_{out}$  using your DMM. Tabulate your results as:  $V_{in}$ ,  $R_L$ ,  $V_{out}$ ,  $I_L$  (in mA). ( $I_L = V_{out} / R_L$ )
4. Calculate output resistance of LM7805 as:  $|\Delta V_{out} / \Delta I_L|$ , where  $\Delta V_{out}$  is the variation in  $V_{out}$  corresponding to the minimum and maximum values of  $I_L$ .
5. Compare the output resistance value you obtained above with that of the bridge rectifier with  $C = 1000\text{ }\mu\text{F}$ . Which is a better DC supply? Justify your answer.
6. Refer to the Datasheet of LM 7805 IC (see the ‘Electrical Characteristics’ on page 2) and note the various parameters of the IC. In particular, note down the specified line regulation, load regulation and the output resistance.

Note: Since variations in  $V_{out}$  will be very small (in the mV range), your DMM may not be able to indicate these minute variations; you will most likely find  $V_{out}$  to be a constant for all values of  $R_L$ .